

DIGITAL : CLOCK



BY
DR . MOHAMED HAMDY



TEAM MEMBERS



AHMED SAYED
POWER



ZIAD ESSAM
COMMUNICATION



MARWA YAHIA
COMMUNICATION




YAHIA RAMADAN
COMMUNICATION



GENERAL IDEA

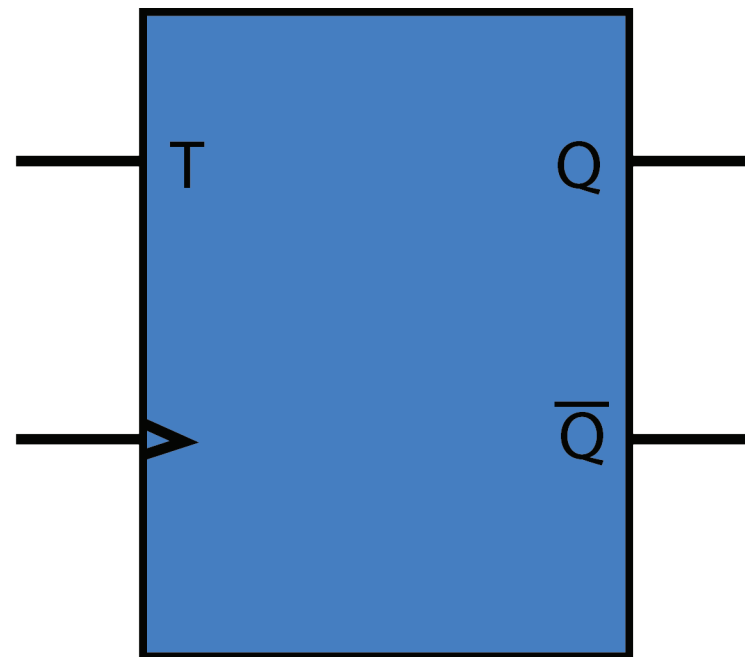MANUFACTURING A DIGITAL CLOCK USING A FLIP FLOP T-TYPE



STEPS






SECONDS “ONES”

MANUFACTURING 4 FLIP FLOP T-TYPE
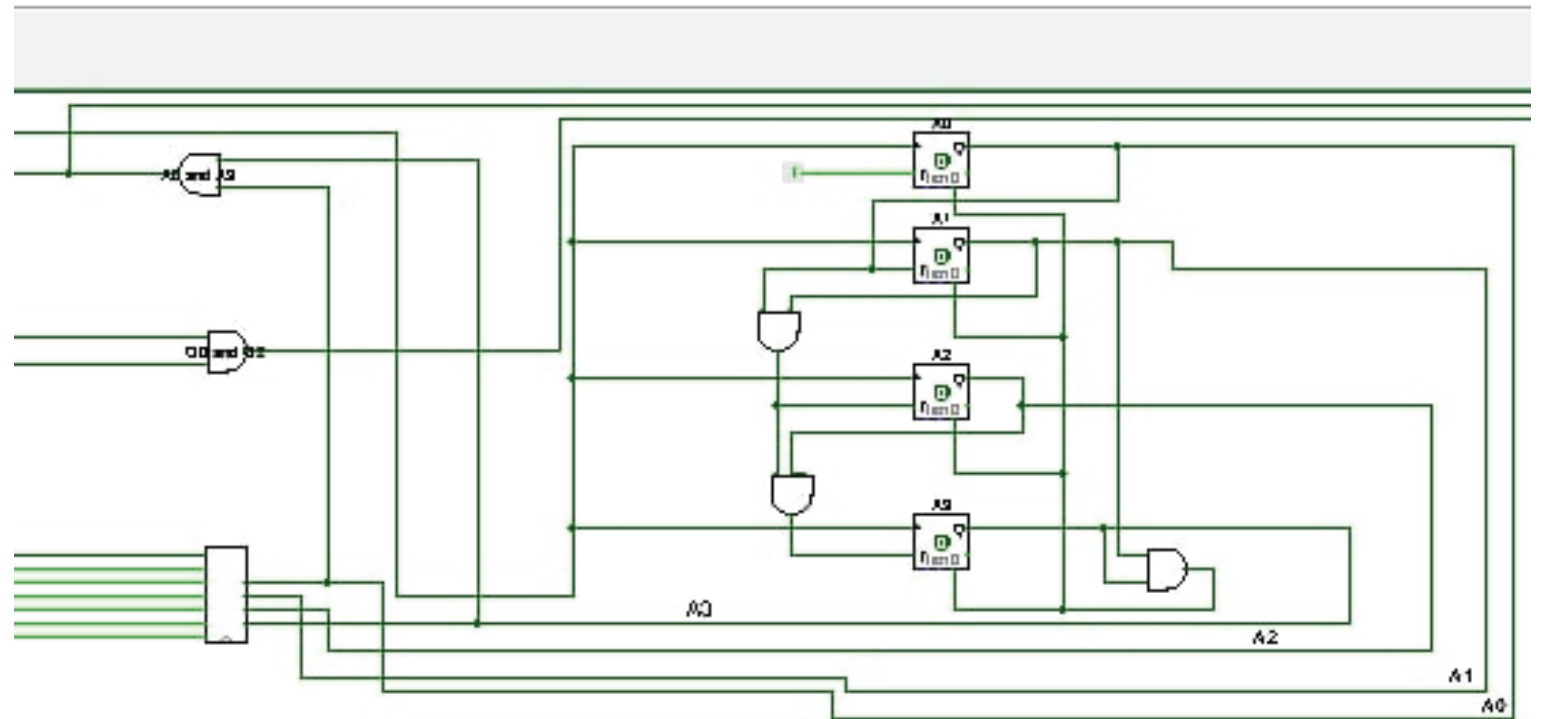
$$T_{o_{\text{stage}}} = T_{o_{\text{stage before}}} * \text{OUT}_{\text{stage before}}$$



THEY HAVE 4 INPUTS:

T_0 T_1 T_2 T_3

AND HAVE 4 OUTPUTS:

A_0 A_1 A_2 A_3



AS:

$$T_0 = 1$$

$$T_1 = A_0 \text{ “} T_0 \text{”}$$


$$T_2 = A_0 A_1 \text{ “} T_0 \text{”}$$

$$T_3 = A_0 A_1 A_2 \text{ “} T_0 \text{”}$$

DO A RESET FROM NUMBER 10 THROUGH CONNECTING THE AND OUTPUT A1 AND A3 TOGETHER USING AND GATE.



STATE DIAGRAM

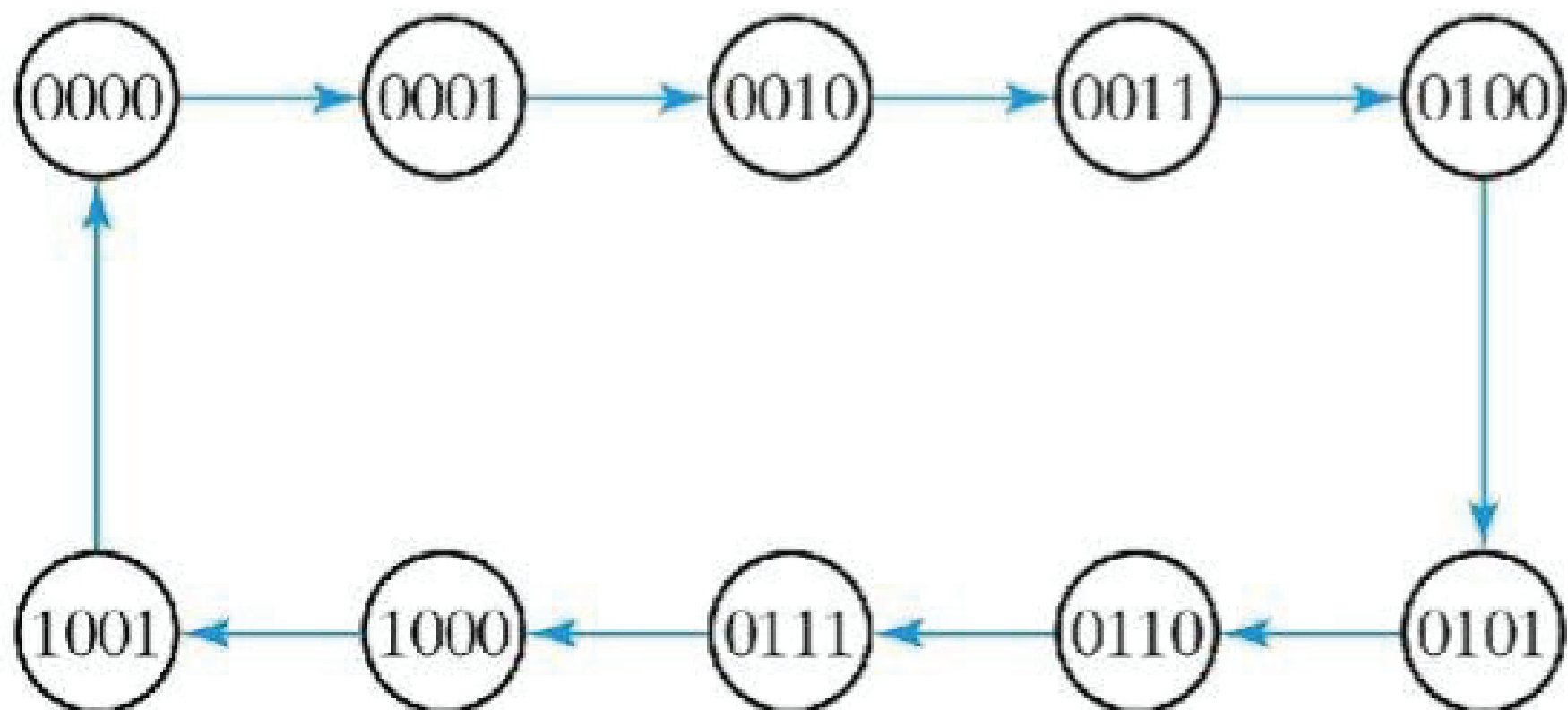




7 SEGMENT

USING THE OUTPUTS OF THE BUILDBOX TO GET THE BOOLEAN FUNCTIONS OF EACH SEGMENTS OF THE 7 SEGMENT. SO IN ORDER TO DISPLAY THE NUMBER “3” FOR EXAMPLE, SEGMENTS A, B, C, D AND G WOULD NEED TO BE ILLUMINATED. IF WE WANTED TO DISPLAY A DIFFERENT NUMBER OR LETTER THEN A DIFFERENT SET OF SEGMENTS WOULD NEED TO BE ILLUMINATED.



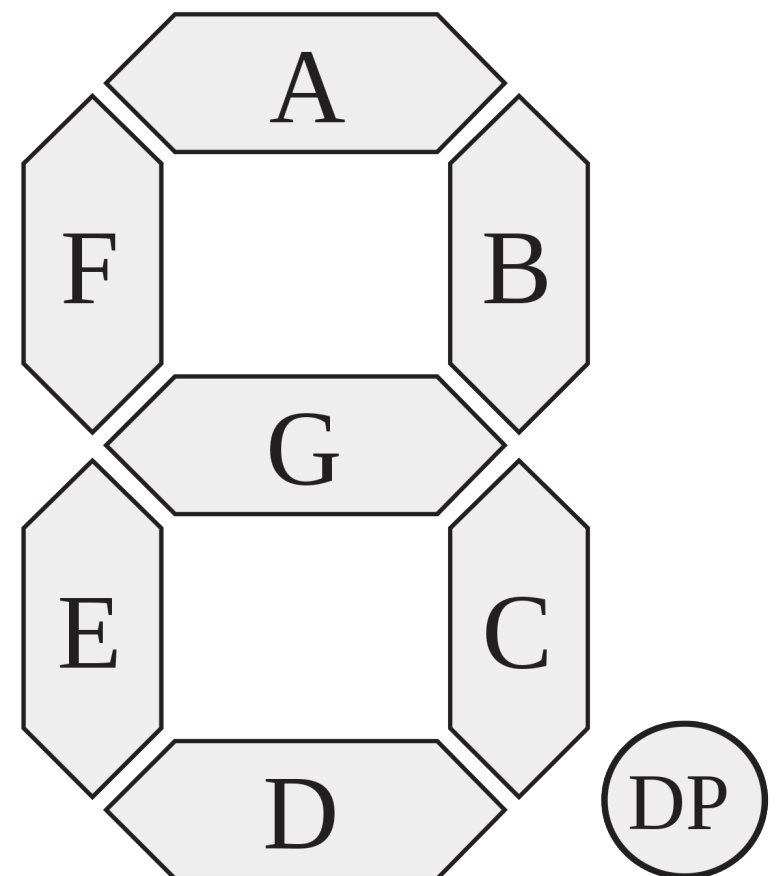7-Segment Display Elements for all Numbers.





7 SEGMENT K-MAPS

Output:

A

Format:

Sum of products

		A1, A0			
		00	01	11	10
A3, A2	00	1	0	1	1
	01	0	1	1	1
	11	x	x	x	x
	10	1	1	x	x

$$\overline{A2} \overline{A0} + A1 + A2 A0 + A3$$

Output:

B

Format:

Sum of products

		A1, A0			
		00	01	11	10
A3, A2	00	1	1	1	1
	01	1	0	1	0
	11	x	x	x	x
	10	1	1	x	x

$$\overline{A2} + \overline{A1} \overline{A0} + A1 A0$$

Output:

C

Format:

Sum of products

		A1, A0			
		00	01	11	10
A3, A2	00	1	1	1	0
	01	1	1	1	1
	11	x	x	x	x
	10	1	1	x	x

$$\overline{A1} + A0 + A2$$



7SEGMENT K-MAPS

Output:

Format:

		A1, A0			
		00	01	11	10
A3, A2	00	1	0	1	1
	01	0	1	0	1
	11	x	x	x	x
	10	1	0	x	x

$$\overline{A2} \overline{A0} + \overline{A2} A1 + A1 \overline{A0} + A2 \overline{A1} A0$$

Output:

Format:

		A1, A0			
		00	01	11	10
A3, A2	00	1	0	0	1
	01	0	0	0	1
	11	x	x	x	x
	10	1	0	x	x

$$\overline{A2} \overline{A0} + A1 \overline{A0}$$

Output:

Format:

		A1, A0			
		00	01	11	10
A3, A2	00	1	0	0	0
	01	1	1	0	1
	11	x	x	x	x
	10	1	1	x	x

$$\overline{A1} \overline{A0} + A2 \overline{A1} + A2 \overline{A0} + A3$$

Output:

Format:

		A1, A0			
		00	01	11	10
A3, A2	00	0	0	1	1
	01	1	1	0	1
	11	x	x	x	x
	10	1	1	x	x

$$\overline{A2} A1 + A2 \overline{A1} + A2 \overline{A0} + A3$$




BCD TO 7 SEGMENT

A3	A2	A1	A0	A	B	C	D	E	F	G
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X



SECONDS “TENS”

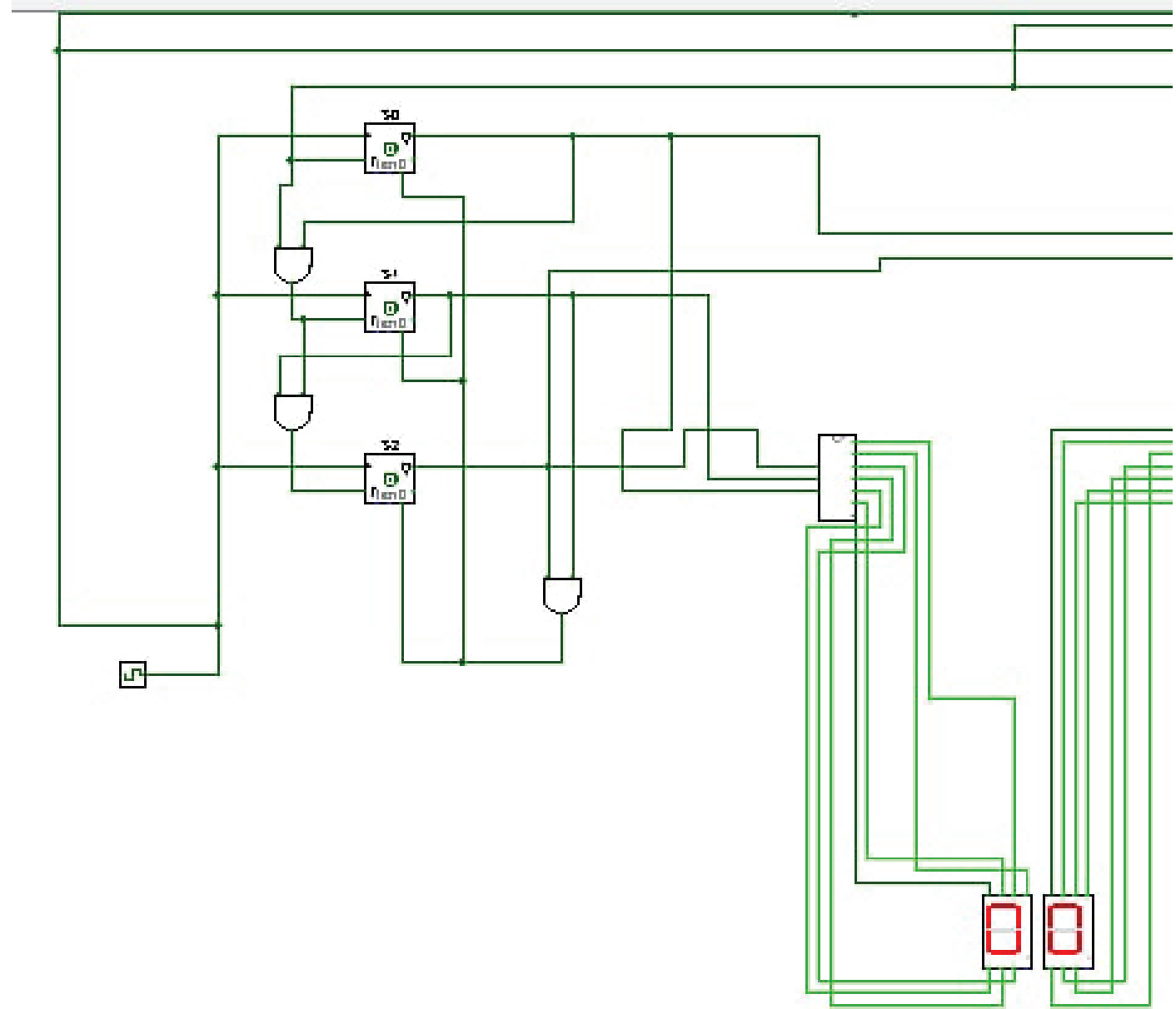

THEY HAVE 3 INPUTS:

T_0 T_1 T_2

AND HAVE 4 OUTPUTS:

Q_0 Q_1 Q_2



AS:


$$T_0 = A_3 A_0$$

$$T_1 = Q_0 T_0$$

$$T_2 = Q_0 Q_1 T_0$$



STATE DIAGRAM

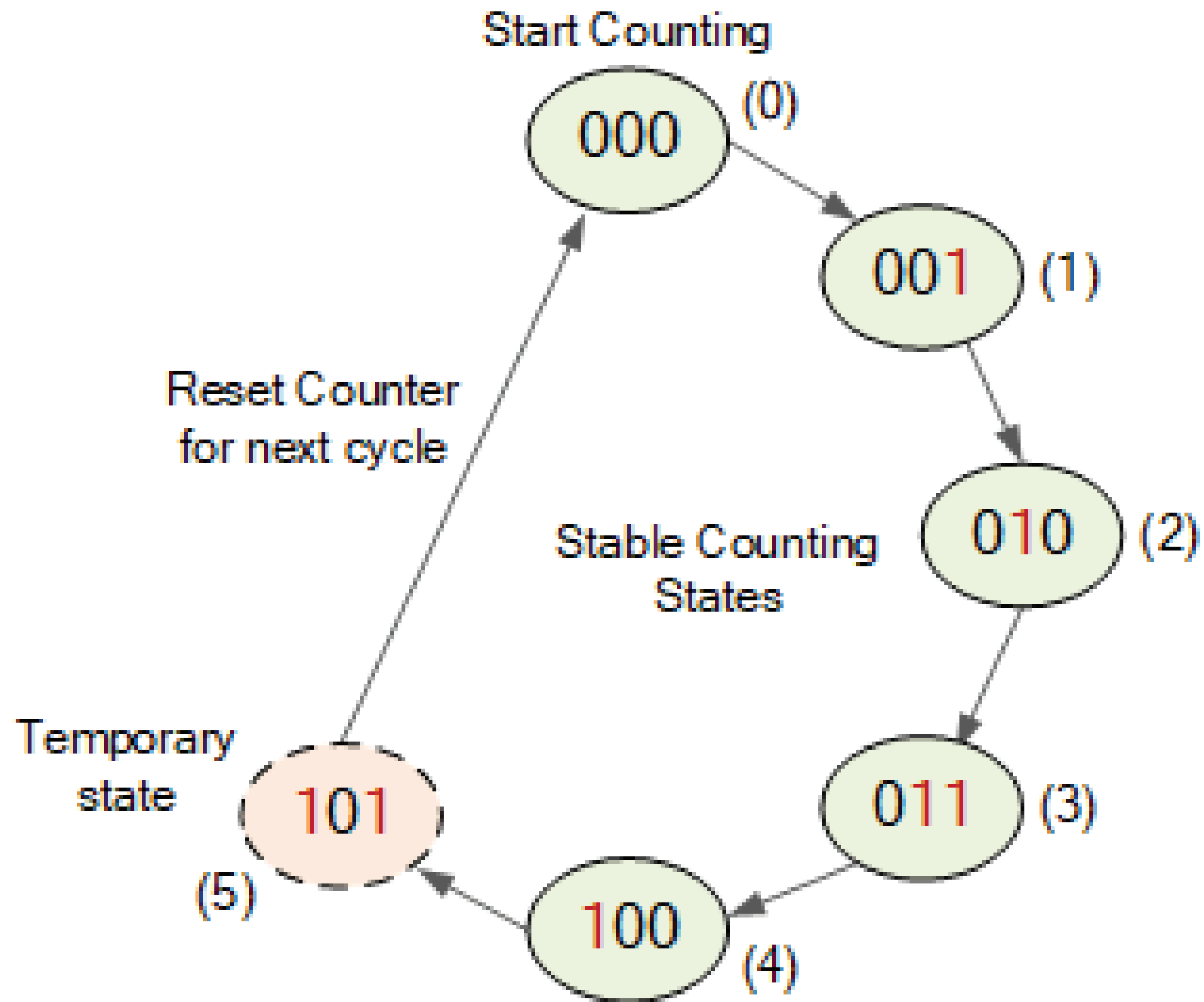



7 SEGMENT K-MAPS

Output:

A

Format:

Sum of products

		Q1, Q0			
		00	01	11	10
Q2	0	1	0	1	1
	1	0	1	1	1

$$\overline{Q_2} \overline{Q_0} + Q_1 + Q_2 Q_0$$

Output:

B

Format:

Sum of products

		Q1, Q0			
		00	01	11	10
Q2	0	1	1	1	1
	1	1	0	1	1

$$\overline{Q_2} + \overline{Q_0} + Q_1$$

Output:

C

Format:

Sum of products

		Q1, Q0			
		00	01	11	10
Q2	0	1	1	1	0
	1	1	1	1	1

$$\overline{Q_1} + Q_0 + Q_2$$

Output:

D

Format:

Sum of products

		Q1, Q0			
		00	01	11	10
Q2	0	1	0	1	1
	1	0	1	1	1

$$\overline{Q_2} \overline{Q_0} + Q_1 + Q_2 Q_0$$



7 SEGMENT K-MAPS

Output:

Format:

Sum of products

		Q1, Q0			
		00	01	11	10
Q2	0	1	0	0	1
	1	0	0	1	1

$$\overline{Q2} \overline{Q0} + Q2 Q1$$

Output:

Format:

Sum of products

		Q1, Q0			
		00	01	11	10
Q2	0	1	0	0	0
	1	1	1	1	1

$$\overline{Q1} \overline{Q0} + Q2$$

Output:

Format:

Sum of products

		Q1, Q0			
		00	01	11	10
Q2	0	0	0	1	1
	1	1	1	1	1

$$Q1 + Q2$$



BCD TO 7 SEGMENT

Q2	Q1	Q0	A	B	C	D	E	F	G
0	0	0	1	1	1	1	1	1	0
0	0	1	0	1	1	0	0	0	0
0	1	0	1	1	0	1	1	0	1
0	1	1	1	1	1	1	0	0	1
1	0	0	0	1	1	0	0	1	1
1	0	1	1	0	1	1	0	1	1
1	1	0	x	x	x	x	x	x	x
1	1	1	x	x	x	x	x	x	x



MINUTES "ONES & TENS"

WE WILL TAKE THE NEXT OUTPUT FROM SECONDS ONES AND TENS . IN ORDER TO GET THE TENS MINUTES, WE ADD A_0 AND A_3 BY USING AND GATE WITH THE OUTPUT COMING FROM MINUTES ONES.


WE NOTE THAT THE MINUTES ONES AND TENS HAVE THE SAME STATE DIGARAM AND THE SAME K-MAPS AS IN SECONDS ONES AND TENS





HOURS “ONES & TENS”

MANUFACTURING 4 FLIP FLOP T-TYPE

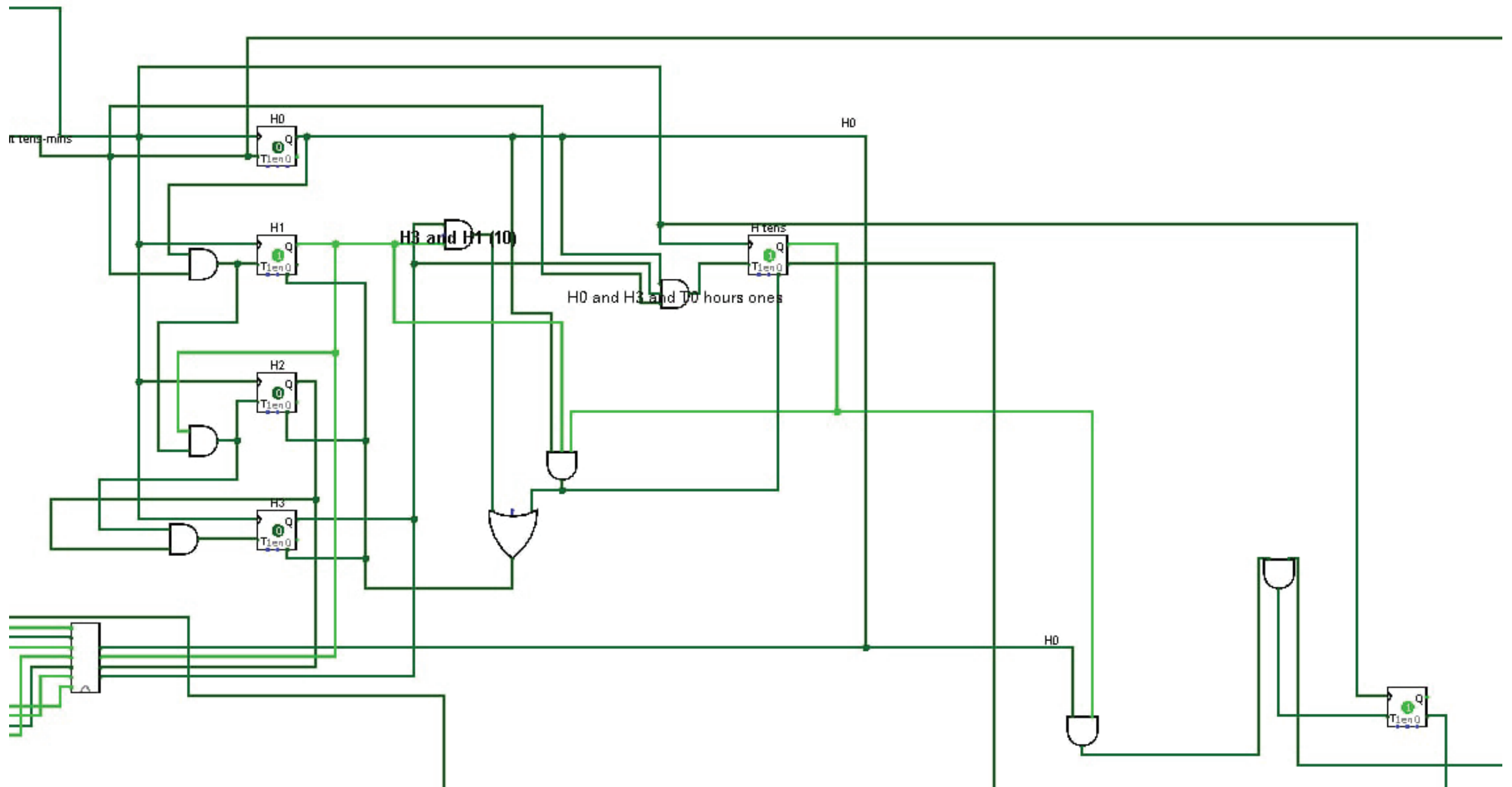



BCD TO 7 SEGMENT

H3	H2	H1	H0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	1	1	0	1	1	1	1
1	0	1	1	1	1	1	1	0	1	1
1	1	0	0	1	1	1	0	0	1	1
1	1	0	1	1	0	1	1	0	1	1
1	1	1	0	1	0	1	1	1	1	1
1	1	1	1	1	1	1	0	0	1	1



7 SEGMENT K-MAPS

Output:

a

Format:

Sum of products

		H1, H0			
		00	01	11	10
H3, H2	00	1	0	1	1
	01	0	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$\overline{H2} \overline{H0} + H1 + H2 H0 + H3$$

Output:

b

Format:

Sum of products

		H1, H0			
		00	01	11	10
H3, H2	00	1	1	1	1
	01	1	0	1	0
	11	1	0	1	0
	10	1	1	1	1

$$\overline{H2} + \overline{H1} \overline{H0} + H1 H0$$

Output:

c

Format:

Sum of products

		H1, H0			
		00	01	11	10
H3, H2	00	1	1	1	0
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	0

$$\overline{H1} + H0 + H2$$

Output:

d

Format:

Sum of products

		H1, H0			
		00	01	11	10
H3, H2	00	1	0	1	1
	01	0	1	0	1
	11	0	1	0	1
	10	1	0	1	1

$$\overline{H2} \overline{H0} + \overline{H2} H1 + H1 \overline{H0} + H2 \overline{H1} H0$$



7 SEGMENT K-MAPS

Output:

Format:

Sum of products

		H1, H0			
		00	01	11	10
H3, H2	00	1	0	0	1
	01	0	0	0	1
	11	0	0	0	1
	10	1	0	0	1

$$\overline{H2} \overline{H0} + H1 \overline{H0}$$

Output:

Format:

Sum of products

		H1, H0			
		00	01	11	10
H3, H2	00	1	0	0	0
	01	1	1	0	1
	11	1	1	1	1
	10	1	1	1	1

$$\overline{H1} \overline{H0} + H2 \overline{H1} + H2 \overline{H0} + H3$$

Output:

Format:

Sum of products

		H1, H0			
		00	01	11	10
H3, H2	00	0	0	1	1
	01	1	1	0	1
	11	1	1	1	1
	10	1	1	1	1

$$\overline{H2} H1 + H2 \overline{H1} + H2 \overline{H0} + H3$$



AM & PM

WHEN WE WANT TO CHANGE BETWEEN, PM AND AM, WE NEED 7 SEGMENT, AND IT WILL BE ON P BY DEFAULT, AND IN ORDER TO CHANGE THE MODE FROM PM TO AM, THE OUTPUT COMING FROM THE HOUR MUST BE EQUAL TO 11:59:59, THEN THE P WILL CHANGE TO A.





SOURCES

DR. MOHAMED HAMDY LECUTURES

**LOGIC AND COMPUTER DESIGN FUNDAMENTALS
5TH ED BY MORRIS R. MANO, CHARLES R. KIME**

**THANK
YOU!!**